

Laplace Transforms

$$f(t) \rightarrow \bar{f}(s), \text{ where } s = \sigma + j\omega$$

complex number $\sqrt{-1}$ imaginary part
real part


- Complex Number Representation
 - $\alpha + \beta j \rightarrow$ Binomial Representation
 - $(\alpha, \beta) \rightarrow$ Cartesian Representation
 - $\sqrt{\alpha^2 + \beta^2} \angle \tan^{-1}(\frac{\beta}{\alpha}) = \sqrt{\alpha^2 + \beta^2} \cdot e^{j \tan^{-1}(\frac{\beta}{\alpha})} \rightarrow$ Polar Representation

- Euler's Identity: $e^{jx} = \cos x + j \sin x$
- Conjugate: $(\alpha + \beta j)^* = \alpha - \beta j$

Inductor Laplace Transform

$$v(t) = L i'(t) \rightarrow V(s) = L s I(s) - L i_c(0)$$


$\hookrightarrow Z_L = L s$

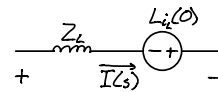

Capacitor Laplace Transform

$$v(t) = \frac{1}{C} \int i(t) dt \rightarrow V(s) = \frac{V_c(0)}{s} + \frac{1}{C s} \int_{-\infty}^{\sigma} i_c(t) dt$$

$\hookrightarrow Z_c = \frac{1}{C s}$

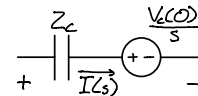

Solving Method

1. Find I.C.: $i_L(0), V_c(0)$

• Assume **steady state** for $t < 0$

• After $t = 0$, circuit enters **Laplace Domain** $\rightarrow$ apply capacitor/inductor Laplace transforms

Phasors

- A Phasor is a complex number representing a sinusoid
- The function $f(t) = A \cos(\omega t + \alpha)$ can be represented by the phasor:

$$\underline{F} = \left(\frac{A}{\sqrt{2}} \right) \angle \alpha$$

Peak Value (V_m / I_m)
RMS Value (V_{rms} / I_{rms})

• Phasor magnitude is **RMS** value; Sinusoid magnitude is **Peak** value


- Phasor voltage/current in **inductor**: $\underline{V}_L = j\omega L \underline{I}$; $\underline{I} = I \angle \alpha$; $Z_L = j\omega L$
- Phasor voltage/current in **capacitor**: $\underline{V}_C = \frac{\underline{I}}{j\omega C}$; $\underline{I} = I \angle \alpha$; $Z_C = \frac{1}{j\omega C}$
- If there are sources with different frequencies, solve for each source, then summate time domain sinusoids (superposition)
- Impedances:

$$Z_L = j\omega L = jX_L \quad Z_C = \frac{-j}{\omega C} = -jX_C \quad Z_R = R$$

- Active Power: electrical power consumed by resistance (R)


$$P_{ac} = \frac{1}{T} \int_0^T v(t) \cdot i(t) dt = \frac{1}{R} \cdot \frac{1}{T} \int_0^T v^2(t) dt = R \cdot \frac{1}{T} \int_0^T i^2(t) dt$$

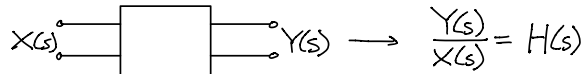Transfer Function: $h(t) \rightarrow H(s)$



- Assume Initial Conditions to compute
- Usually written as a ratio of polynomials of " s "
- Roots in numerator of transfer function result in zeros
 - HP-Prime "root(num(H(s)))"
- Roots in denominator of transfer function result in poles
 - HP-Prime "root(denom(H(s)))"
- Stability
 - $h(t) = u(t)e^{-\alpha t} \xrightarrow{L} \frac{1}{s+\alpha} = H(s)$
 - Stable if root is less than 0

Complex Plane

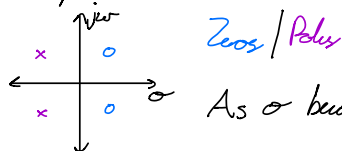


As σ becomes more negative, system decays faster: $e^{-\alpha t} = \frac{1}{s+\alpha}$

- Decibel conversion ($20 \log_{10} |Y(s)|$) to apply transfer function:

$$20 \log_{10} |Y(s)| = 20 \log_{10} |H(s)| + 20 \log_{10} |X(s)|$$

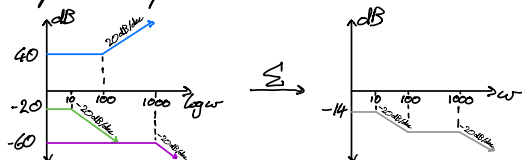- Graphed Representation: Ex: $H(s) = \frac{2(s+100)}{(s+10)(s+1000)}$



Bode Plots


- decibels as a function of frequency: Exact $dB = 20 \log_{10} |H(j\omega)|$
- $$H(s) = \frac{a_n s^n + a_{n-1} s^{n-1} + \dots + a_1 s + a_0}{s^m + b_{m-1} s^{m-1} + \dots + b_1 s + b_0} = \frac{(s+z_1)(s+z_2)\dots(s+z_{n-1})}{(s+p_1)(s+p_2)\dots(s+p_m)}$$
- Represent as ratio of polynomials, or zeros and poles
 - Treat $(s-a)$ as $(s+\alpha)$ $\rightarrow$ same contribution to dB Bode plot

$$H(s) = \frac{A s (\frac{s}{z_1} + 1) (\frac{s}{z_2} + 1) \dots (\frac{s}{z_{n+1}} + 1)}{(\frac{s}{p_1} + 1) (\frac{s}{p_2} + 1) \dots (\frac{s}{p_m} + 1)} ; \lim_{s \rightarrow \infty} H(s) = A$$


- Plot will be shifted up by: $\alpha_{dB} = 20 \log_{10} A$
- A "bend" (zero or pole) will have maximum error of 3dB, with $\pm 20 \text{ dB/dec}$
 - A higher order bend: $(s+p_i)^n$; $n > 1$ will have maximum error of $n \cdot 3 \text{ dB}$, with $\pm n \cdot 20 \text{ dB/dec}$
- Zero at zero $\rightarrow 0 \text{ dB @ } \omega = 1 \text{ rad/sec}$



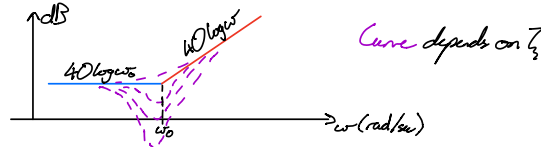- Complex Conjugate: $(s^2 + 2\zeta\omega_c s + \omega_c^2) \rightarrow \text{contributor: } \alpha_{dB} = \sqrt{(\omega_c^2 - \omega^2)^2 + (2\zeta\omega_c\omega)^2}$
 - at high frequencies; $\omega \gg \omega_c$: $\alpha_{dB} \approx 40 \log_{10} \omega$
 - at low frequencies; $\omega \ll \omega_c$: $\alpha_{dB} \approx 40 \log_{10} \omega_c$



- phase as a function of frequency: Exact $\Phi = \angle H(j\omega)$
 - Zero/Pole at a contributes $\pm 45^\circ$ at $0.1a$, and $\pm 45^\circ$ at $10a$
 - +ve constant $\rightarrow 0^\circ$ phase shift, -ve constant $\rightarrow -180^\circ$ phase shift
 - Zero/Pole at 0 contributes $\pm 90^\circ$, Treat $(s-a)$ as $s^2/(s+a)$ for phase Bode plot
- Complex Conjugate: $[s-(\sigma+j\omega_d)][s-(\sigma-j\omega_d)] = (s^2 + 2\zeta\omega_c s + \omega_c^2) \xrightarrow{s=j\omega} (\omega_c^2 - \omega^2) + j2\zeta\omega_c\omega$

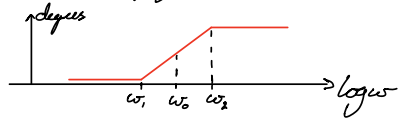

$$\omega_c = \sqrt{\omega_1 \omega_2}$$

$$\omega_1 = \omega_c \cdot 10^{-\zeta}$$

$$\omega_2 = \omega_c \cdot 10^{\zeta}$$

$$\text{slope}_{\omega_1, \omega_2} = \frac{90^\circ}{\zeta}$$

damping factor

$$\text{Exact Complex Conjugate } \Phi = \tan^{-1} \left(\frac{2\zeta\omega_c\omega}{\omega_c^2 - \omega^2} \right)$$


Resonance

- Certain frequency that makes circuit look purely resistive from given port
- Bandwidth: width between half power frequencies
- Quality Factor: $Q = \frac{\omega_c}{BW} = \frac{\omega_c}{\omega_2 - \omega_1}$; $Q \gg 10 \rightarrow$ highly selective filter

resonant frequency

Filters

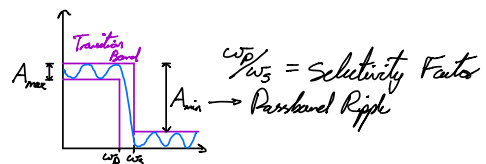- Electric network that blocks unwanted frequencies
- Passband: signals that are allowed
- Stopband: signals that are not allowed



Classification Types

- Low Pass filter: $H(s) = 1/(s+a)$; below certain frequency
- High Pass filter: $H(s) = s/(s+a)$; above certain frequency
- Band Pass filter: $H(s) = s/(s+a)(s+b)$; range of certain frequencies
- Band Stop filter: $H(s) = (s^2 + \omega_N^2)/(s^2 + BW \cdot s + \omega_N^2)$ Null Frequency


Cutoff Frequency (ω_c)

A pole that creates a bend from 0 slope to -ve slope or vice versa

- Defined as ω_c & ω_N — frequencies in which the signal goes up/down 3dB from 0 slope
- Occurs when ω_c : $|H(j\omega_c)| = \frac{1}{\sqrt{2}} |H(j \cdot 0)|$
- Canonical Form: $\omega_c = 1$ rad/s

Butterworth Filter

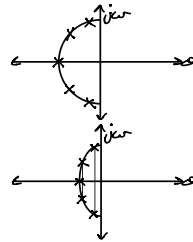- All poles exist on circle around origin



Chebyshev Filter

- All poles exist in pairs, equidistant on ellipse around origin

Magnitude/Frequency Scaling


- Increase resistors/inductors by factor K_m , and shift frequency response by K_f

$$R' = K_m \cdot R \quad L' = \frac{K_m}{K_f} \cdot L \quad \omega' = K_f \cdot \omega$$

$$C' = \frac{C}{K_m \cdot K_f}$$


RLC Circuit
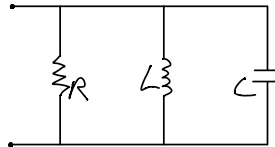
$$\omega_0 = \frac{1}{\sqrt{LC}}, \quad Q = \omega_0 \cdot RC$$



Two Port Network

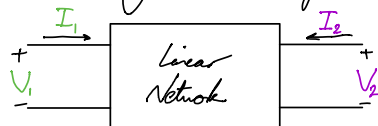- Characterized by two voltages and two currents $\rightarrow$ two as inputs/two as outputs



Impedance Parameters ($Z = \frac{V}{I}$)

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$Z_{11} = \frac{V_1}{I_1} \quad Z_{21} = \frac{V_2}{I_1}$$

$$Z_{12} = \frac{V_1}{I_2} \quad Z_{22} = \frac{V_2}{I_2}$$

- Network is **Symmetric** if $Z_{11} = Z_{22}$
- Network is **Reciprocal** if $Z_{12} = Z_{21}$

• Admittance Parameters ($Y = \frac{I}{V}$)

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$


$$Y_{11} = \frac{I_1}{V_1}$$

$$Y_{12} = \frac{I_1}{V_2}$$

$$Y_{21} = \frac{I_2}{V_1}$$

$$Y_{22} = \frac{I_2}{V_2}$$

• Models of Network Cases

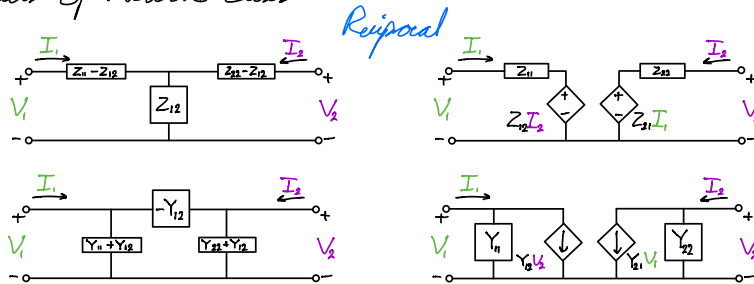

• Hybrid Parameters (h)


Sometimes networks do not have exclusively admittance or impedance parameters

$$V_1 = h_{11} I_1 + h_{12} V_2$$

Short-circuit input impedance Open-circuit reverse voltage gain

$$I_2 = h_{21} I_1 + h_{22} V_2$$

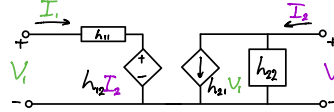Short-circuit forward current gain Open-circuit output admittance




• Transmission Parameters ($T = \begin{bmatrix} A & B \\ C & D \end{bmatrix}$)


$$\begin{aligned} V_1 &= A V_2 - B I_2 \\ I_1 &= C V_2 - D I_2 \end{aligned} \rightarrow \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

• Combine 2 Two Port Networks


Cascade: Matrix Multiply

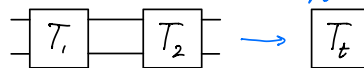

Series: Matrix Addition

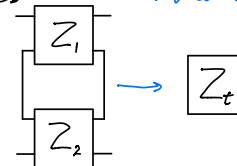

Parallel: Matrix Addition

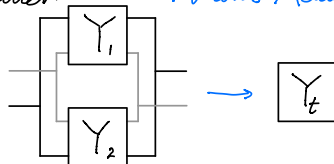

Parameter Conversion Table

to \ from	Z	Y	H	G	T
Z	$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix}$	$\begin{bmatrix} \frac{y_{22}}{\Delta_y} & -\frac{y_{12}}{\Delta_y} \\ -\frac{y_{21}}{\Delta_y} & \frac{y_{11}}{\Delta_y} \end{bmatrix}$	$\begin{bmatrix} \frac{\Delta_h}{h_{22}} & \frac{h_{12}}{h_{22}} \\ -\frac{h_{21}}{h_{22}} & \frac{h_{11}}{h_{22}} \end{bmatrix}$	$\begin{bmatrix} \frac{1}{g_{11}} & -\frac{g_{12}}{g_{11}} \\ \frac{g_{21}}{g_{11}} & \frac{g_{22}}{g_{11}} \end{bmatrix}$	$\begin{bmatrix} \frac{t_{11}}{t_{21}} & \frac{\Delta_t}{t_{21}} \\ \frac{1}{t_{21}} & \frac{t_{22}}{t_{21}} \end{bmatrix}$
Y	$\begin{bmatrix} \frac{y_{22}}{\Delta_y} & -\frac{y_{12}}{\Delta_y} \\ -\frac{y_{21}}{\Delta_y} & \frac{y_{11}}{\Delta_y} \end{bmatrix}$	$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$	$\begin{bmatrix} \frac{1}{h_{11}} & -\frac{h_{12}}{h_{11}} \\ \frac{h_{21}}{h_{11}} & \frac{h_{22}}{h_{11}} \end{bmatrix}$	$\begin{bmatrix} \frac{\Delta_g}{g_{22}} & \frac{g_{12}}{g_{22}} \\ -\frac{g_{21}}{g_{22}} & \frac{g_{11}}{g_{22}} \end{bmatrix}$	$\begin{bmatrix} \frac{t_{22}}{t_{12}} & -\frac{\Delta_t}{t_{12}} \\ \frac{1}{t_{12}} & \frac{t_{11}}{t_{12}} \end{bmatrix}$
H	$\begin{bmatrix} \frac{\Delta_h}{h_{22}} & \frac{h_{12}}{h_{22}} \\ -\frac{h_{21}}{h_{22}} & \frac{h_{11}}{h_{22}} \end{bmatrix}$	$\begin{bmatrix} \frac{1}{y_{11}} & -\frac{y_{12}}{y_{11}} \\ \frac{y_{21}}{y_{11}} & \frac{y_{22}}{y_{11}} \end{bmatrix}$	$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix}$	$\begin{bmatrix} \frac{g_{22}}{\Delta_g} & -\frac{g_{12}}{\Delta_g} \\ -\frac{g_{21}}{\Delta_g} & \frac{g_{11}}{\Delta_g} \end{bmatrix}$	$\begin{bmatrix} \frac{t_{12}}{t_{22}} & \frac{\Delta_t}{t_{22}} \\ \frac{t_{21}}{t_{22}} & \frac{t_{22}}{t_{22}} \end{bmatrix}$
G	$\begin{bmatrix} \frac{1}{g_{11}} & -\frac{g_{12}}{g_{11}} \\ \frac{g_{21}}{g_{11}} & \frac{g_{22}}{g_{11}} \end{bmatrix}$	$\begin{bmatrix} \frac{\Delta_y}{y_{22}} & \frac{y_{12}}{y_{22}} \\ -\frac{y_{21}}{y_{22}} & \frac{y_{11}}{y_{22}} \end{bmatrix}$	$\begin{bmatrix} \frac{h_{22}}{\Delta_h} & -\frac{h_{12}}{\Delta_h} \\ \frac{h_{21}}{\Delta_h} & \frac{h_{11}}{\Delta_h} \end{bmatrix}$	$\begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix}$	$\begin{bmatrix} \frac{t_{21}}{t_{11}} & -\frac{\Delta_t}{t_{11}} \\ \frac{1}{t_{11}} & \frac{t_{12}}{t_{11}} \end{bmatrix}$
T	$\begin{bmatrix} \frac{z_{11}}{z_{21}} & \frac{\Delta_z}{z_{21}} \\ \frac{1}{z_{21}} & \frac{z_{22}}{z_{21}} \end{bmatrix}$	$\begin{bmatrix} -\frac{y_{22}}{\Delta_y} & \frac{1}{\Delta_y} \\ \frac{y_{21}}{\Delta_y} & \frac{y_{11}}{\Delta_y} \end{bmatrix}$	$\begin{bmatrix} -\frac{\Delta_h}{h_{21}} & \frac{h_{11}}{h_{21}} \\ \frac{h_{21}}{h_{21}} & \frac{h_{22}}{h_{21}} \end{bmatrix}$	$\begin{bmatrix} \frac{1}{g_{21}} & \frac{g_{22}}{g_{21}} \\ \frac{g_{21}}{g_{21}} & \frac{g_{22}}{g_{21}} \end{bmatrix}$	$\begin{bmatrix} \frac{t_{11}}{t_{21}} & \frac{t_{12}}{t_{21}} \\ \frac{t_{21}}{t_{21}} & \frac{t_{22}}{t_{21}} \end{bmatrix}$

$$\Delta X = X_{11}X_{22} - X_{12}X_{21}$$

AC Power Analysis

Average Power

$$v(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

- Complex Power = Active Power + $j \cdot$ Reactive Power [VA]


$$S = P + jQ = V_{rms} \cdot I_{rms}^* = I_{rms}^2 \cdot Z$$

$$|S| = V_{rms} \cdot I_{rms} = \sqrt{P^2 + Q^2}$$

$$P = |S| \cos(\theta_v - \theta_i) \text{ [W]}$$

$$Q = |S| \sin(\theta_v - \theta_i) \text{ [VAR]}$$
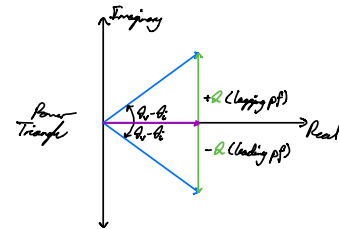
$$\text{Power Factor: } pf = \frac{P}{S} = \cos(\theta_v - \theta_i)$$



- Maximizing Power through Impedance (Z)
 - Thévenin equivalent impedance (Z_{th}) around Z is complex conjugate of impedance value for Z as to draw maximum power:

$$Z = Z_{th}^* = \left(\frac{V_{th}}{i_{sc}} \right)^*$$

- Instantaneous Power [VA]

$$p(t) = v(t)i(t) = \frac{V_m i_m}{2} [\cos(\theta_v - \theta_i) + \cos(2\omega t + (\theta_v + \theta_i))]$$

$$= \frac{V_m i_m}{2} \underbrace{[\cos(\theta_v - \theta_i) \cdot (1 + \cos(2\omega t))]}_{P(t)} + \underbrace{\sin(\theta_v - \theta_i) \cdot \sin(2\omega t)}_{Q(t)}$$



- Power Conservation

Sum of element power of circuit must equal 0


All power have power conservation except for Apparent Power [VA]

Three Phase Circuits

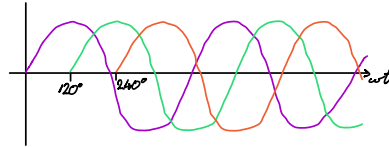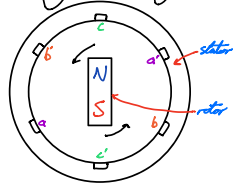- Circuit Network with three sources that are out of phase with each other by 120° , with same amplitude and frequency
- A three phase generator consists of a rotating magnet (rotor) surrounded by a stationary winding (stator)




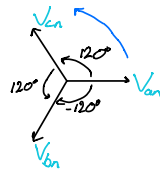- Phase Sequence: time order in which the voltages pass through their maximum values




$$\begin{aligned} V_{an} &= V_p \angle 0^\circ \\ V_{bn} &= V_p \angle -120^\circ \\ V_{cn} &= V_p \angle 120^\circ \end{aligned}$$

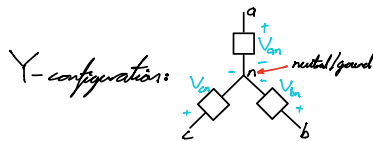- Balanced Three-Phase Voltages are equal in magnitude and out of phase by 120°
- Balanced Load: impedances are equal in magnitude and phase
- Balanced Three-Phase Connections (Source - Load)


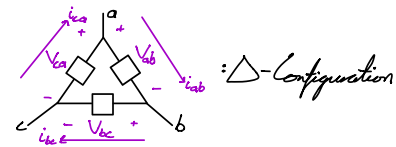
$$3Z_Y = Z_\Delta \quad \text{Convert between Y & } \Delta$$



Y-Y connection

$$\begin{aligned} V_L &= V_p \sqrt{3} \\ V_{an} - V_{bn} &= \sqrt{3} V_p \angle 30^\circ \\ V_{bn} - V_{cn} &= \sqrt{3} V_p \angle -90^\circ \\ V_{cn} - V_{an} &= \sqrt{3} V_p \angle -210^\circ \end{aligned}$$

Phase Voltage

$$\begin{aligned} i_L &= i_p \\ i_a &= V_{an} / Z_Y \\ i_b &= V_{bn} / Z_Y \\ i_c &= V_{cn} / Z_Y \end{aligned} \quad i_a + i_b + i_c = 0$$

Phase Current

$$V_L = |V_{ab}| + |V_{bc}| + |V_{ca}|$$

$$V_p = |V_{an}| + |V_{bn}| + |V_{cn}|$$

Y-Δ connection

$$\begin{aligned} i_L &= i_p \sqrt{3} \\ V_L &= V_p \\ i_{ab} &= V_{ab} / Z_\Delta \\ i_{bc} &= V_{bc} / Z_\Delta \\ i_{ca} &= V_{ca} / Z_\Delta \end{aligned}$$

$$i_L = |i_a| + |i_b| + |i_c|$$

$$i_p = |i_{ab}| + |i_{bc}| + |i_{ca}|$$

Δ-Δ & Δ-Y connections

- Convert these configurations to Y-Y

$$\begin{aligned} V_{ab} &= V_L \\ V_{bc} &= V_L \angle -120^\circ \\ V_{ca} &= V_L \angle 120^\circ \end{aligned}$$

$$\begin{aligned} V_{an} &= V_L / \sqrt{3} \angle -30^\circ \\ V_{bn} &= V_L / \sqrt{3} \angle -150^\circ \\ V_{cn} &= V_L / \sqrt{3} \angle 90^\circ \end{aligned}$$

Unbalanced Three-Phase Connections

• Y-Y connection

$$\begin{aligned} i_a &= V_{an}/Z_a \\ i_b &= V_{bn}/Z_b \\ i_c &= V_{cn}/Z_c \end{aligned}$$

$$i_a + i_b + i_c + i_n = 0$$

Instantaneous Power ($Z_Y = Z \angle \theta$)

$$\begin{aligned} V_{an}(t) &= V_p \sqrt{2} \cos(\omega t) \\ i_a(t) &= i_p \sqrt{2} \cos(\omega t - \theta) \end{aligned}$$

$$P_a(t) = 2 V_p i_p \cos(\omega t) \cos(\omega t - \theta)$$

$$P(t) = P_a(t) + P_b(t) + P_c(t) = 3 V_p i_p \cos \theta$$

• Instantaneous Power as a function of time is a constant

Power per Phase

• Average: $P_p = V_p i_p \cos \theta$

• Reactive: $Q_p = V_p i_p \sin \theta$

• Apparent: $|S_p| = V_p i_p$

• Complex: $S_p = V_p i_p \angle \theta = P_p + j Q_p = V_p \cdot i_p^*$

$$S_L = 3 i_L^2 \cdot Z_Y \angle \theta_{ZY}$$

Total Power

• Average: $P = 3 P_p = 3 V_p i_p \cos \theta = \sqrt{3} V_L i_L \cos \theta$


• Reactive: $Q = 3 Q_p = 3 V_p i_p \sin \theta = \sqrt{3} V_L i_L \sin \theta$

• Apparent: $|S| = 3 |S_p| = 3 V_p i_p = \sqrt{3} V_L i_L$

• Complex: $S = 3 S_p = 3 V_p i_p \angle \theta = \sqrt{3} V_L i_L \angle \theta = P + j Q = 3 V_p \cdot i_p^*$


Power Loss

• Single-Phase System

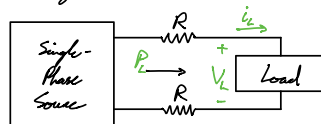

$$P_{\text{loss}} = 2R \frac{P_L^2}{V_L^2}$$

• Three-Phase System

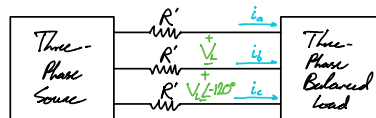

$$P_{\text{loss}} = R' \frac{P_L^2}{V_L^2}$$


• Three-Phase systems have much lower power loss

Magnetically Coupled Circuits

• Self-Inductance

- Current passing through coil generates magnetic flux through it
- A voltage is induced across the coil when flux changes
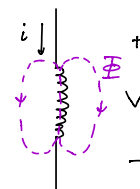
$$V = N \frac{d\Phi}{dt} = N \frac{d\Phi}{di} \cdot \frac{di}{dt} = L \frac{di}{dt} \rightarrow L = N \frac{d\Phi}{di}$$




• Mutual-Inductance

- Change in magnetic flux may result from nearby coil

$$\Phi = \Phi_1 + \Phi_2$$

$$V_1 = N_1 \frac{d\Phi_1}{dt} \quad V_2 = N_2 \frac{d\Phi_2}{dt} = M_{21} \frac{di_1}{dt}$$

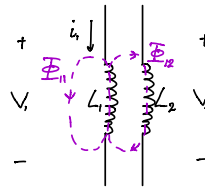
$$M_{21} = N_2 \frac{d\Phi_{12}}{dt} [\text{Henry}]$$



- Mutual-Inductance is the ability of one inductor to induce a voltage across a nearby inductor

• Dot Convention

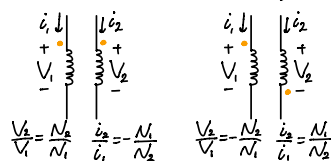
- indicates polarity of mutual-inductance voltage




Dots on same side: $\hat{V}_1 = \hat{V}_2 \quad \hat{i}_1 = -\hat{i}_2$

Dots on opposite side: $\hat{V}_1 = -\hat{V}_2 \quad \hat{i}_1 = \hat{i}_2$

• Coupled Coils in Series

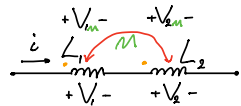
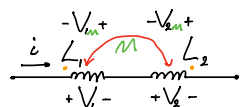
$$L_T = L_1 + L_2 + 2M \rightarrow \text{Series Aiding Connection}$$



$$L_T = L_1 + L_2 - 2M \rightarrow \text{Series Opposing Connection}$$

• Energy in Coupled Circuits

$$W = \frac{L_1 i_1^2}{2} + \frac{L_2 i_2^2}{2} + M i_1 i_2$$

if dots are on same side
if dots are on opposite side

• Energy Conservation bounds Mutual-Inductance

$$M \leq \sqrt{L_1 L_2} \rightarrow K = \frac{M}{\sqrt{L_1 L_2}} = \frac{\Phi_{12}}{\Phi_1 + \Phi_2}; \quad 0 \leq K \leq 1$$

No magnetic flux crossover
Maximum magnetic flux crossover

- K is a measure of how much magnetic flux passes from one coil to the other


• Ideal Transformer

- Unity-coupled, lossless transformer with infinite self-inductances

$$K=1$$

$$R_1 = R_2 = \infty$$

$$L_1 = L_2 = \infty$$

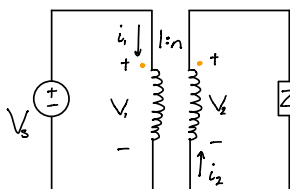

$$n = \frac{N_2}{N_1}$$

ratio of number of turns of inductors


$$\frac{V_2}{V_1} = \frac{N_2}{N_1}$$

$$\frac{i_2}{i_1} = \frac{N_1}{N_2}$$

$$V_2 > V_1 \rightarrow \text{step-up transformer}$$

$$V_2 < V_1 \rightarrow \text{step-down transformer}$$


Equivalent Circuit

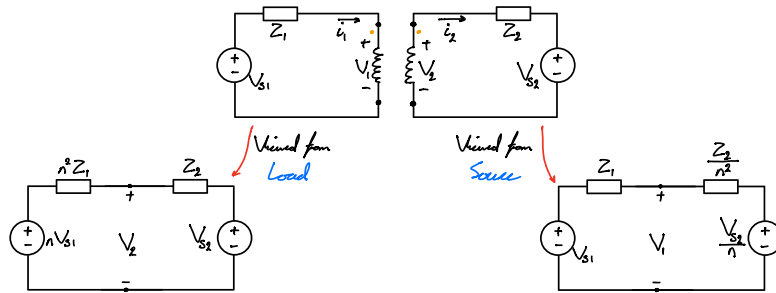

Second-Order Circuit

- A circuit characterized by a **Second-Order Differential Equation**
- Consists of 2 energy storage elements

RLC Circuit

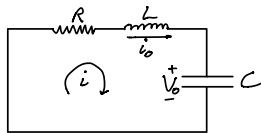

$$Ri + L \frac{di}{dt} + \frac{1}{C} \int_{-\infty}^t i dt = 0 \rightarrow \text{KVL Equation}$$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0 \rightarrow \text{Second-Order Differential Equation}$$

$$S_1 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$S_2 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \rightarrow \text{Characteristic Equation}$$

$$\alpha = \frac{R}{2L} \rightarrow \text{Damping Factor}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \rightarrow \text{Resonance Frequency}$$

Solutions of Characteristic Equation (**Transient Response**)

Overdamped: $\alpha > \omega_0 \rightarrow i(t)/v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$ Determined by Initial Conditions

Critically Damped: $\alpha = \omega_0 \rightarrow i(t)/v(t) = (A_1 t + A_2) e^{-\alpha t}$

Underdamped: $\alpha < \omega_0 \rightarrow i(t)/v(t) = A_1 e^{-(\alpha - j\omega_d)t} + A_2 e^{-(\alpha + j\omega_d)t}$
 $= e^{-\alpha t} [(A_1 + A_2) \cos(\omega_d t) + j(A_1 - A_2) \sin(\omega_d t)]$

$$S_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -\alpha \pm j\sqrt{\omega_0^2 - \alpha^2} = -\alpha \pm j\omega_d$$
 damping frequency

Steady-State Response: $V_{ss} = V(\infty) = V_s$ / $i_{ss} = i(\infty) = 0$

Complete Solution = **Steady-State Response** + **Transient Response**

Method to finding solution of second order circuits

- Transient Response** by turning off independent sources
- Steady-State Response** by finding final state